



[Date]


[Project 1]

[Spartan6 - DSP48A1]




Mohamed Lotfy

1.DSP48A1 Block:

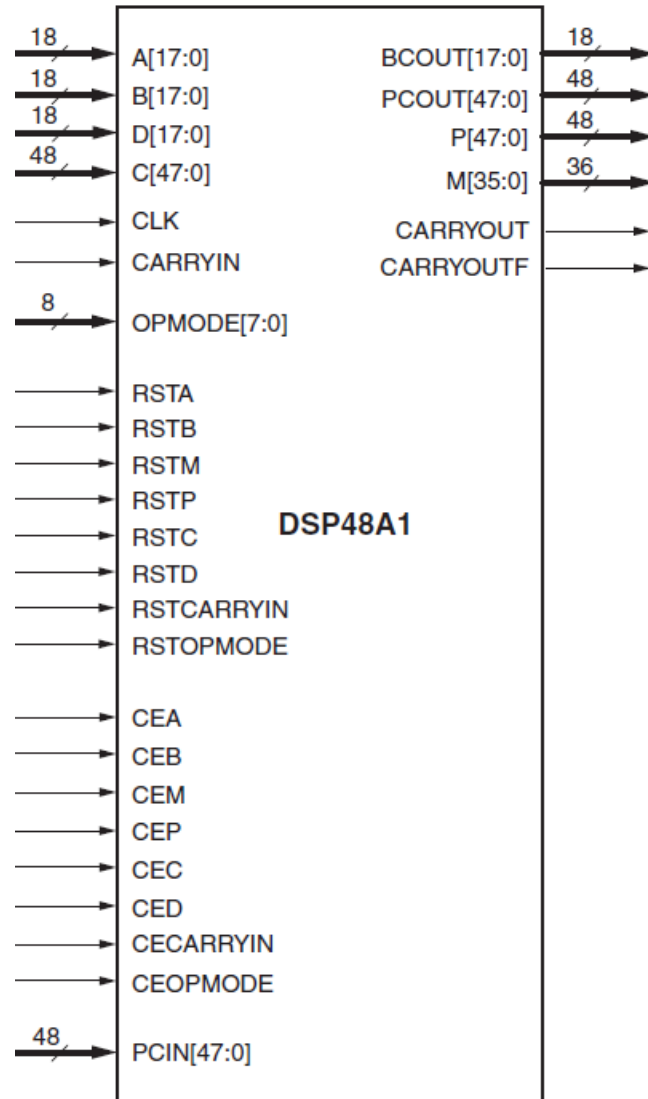

2. Internal Design:

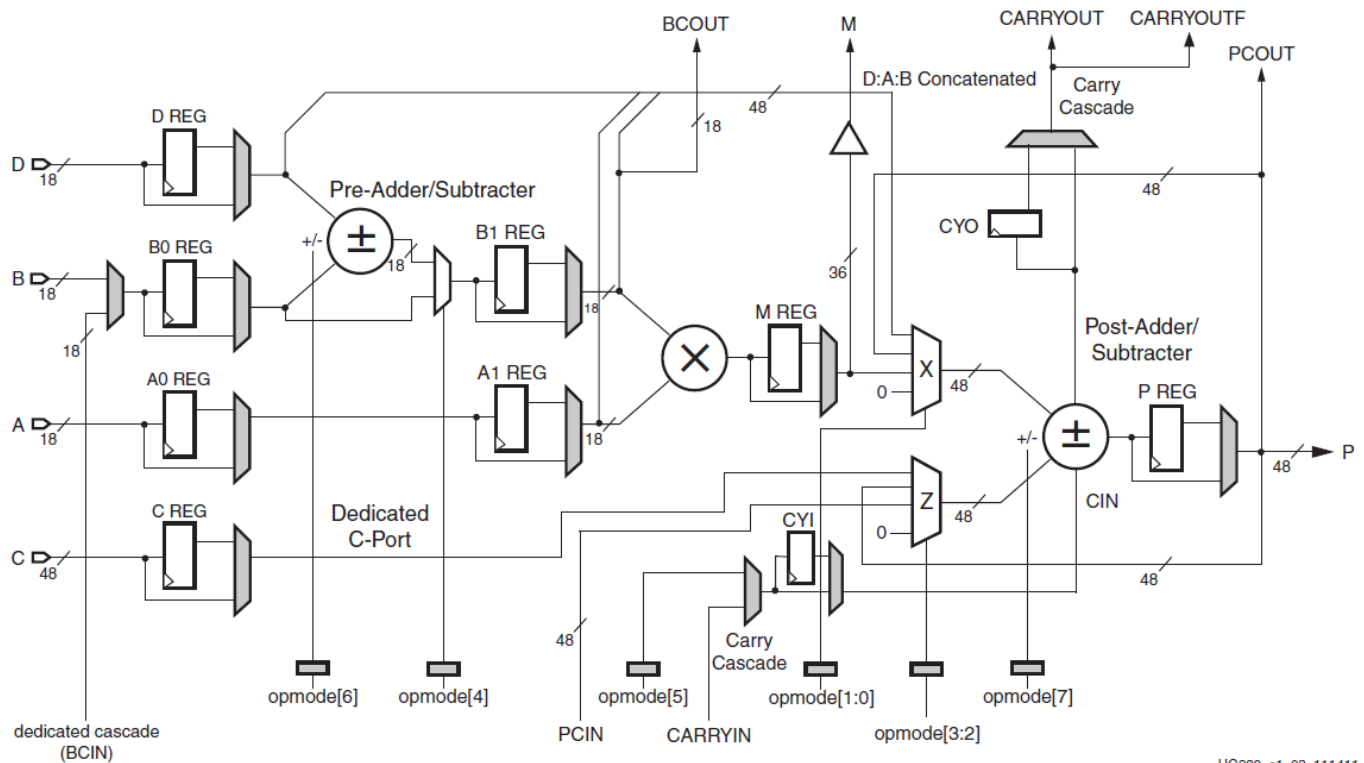

UG389_c1_03_111411

3.Verilog Code:

- Small Module:

```
module Reg_Mux (sel,in,clk,enable,rst,out);
parameter width = 1;
parameter RSTTYPE = "ASYNC";
input [width-1:0] in;
input sel,clk,rst,enable;
output [width-1:0] out;
reg [width-1:0] out_reg;

generate
    if(RSTTYPE == "SYNC" )begin
        always @(posedge clk) begin
            if(rst)begin
                out_reg <=0;
            end
            else if(enable)begin
                out_reg <= in;
            end
        end
    end
    else if(RSTTYPE == "ASYNC")begin
        always @(posedge clk , posedge rst) begin
            if(rst)begin
                out_reg <=0;
            end
            else if(enable) begin
                out_reg <= in;
            end
        end
    end
endgenerate
assign out = (sel==1)?out_reg:in;
endmodule
```

- RTL Code:

```

module DSP48A1 (A,B,C,D,CARRYIN,M,P,CARRYOUT,CARRYOUTF,CLK,OPMODE,
CEA,CEB,CEC,CED,CECARYIN,CEM,CEOPMODE,CEP,RSTA,RSTB,RSTC,RSTD
,RSTM,RSTCARRYIN,RSTOPMODE,RSTP,PCIN,BCIN,BCOUT,PCOUT);
// DEFINE PARAMETERS
parameter A0REG =0;
parameter A1REG =1;
parameter B0REG =0;
parameter B1REG =1;
parameter CREG =1;
parameter DREG =1;
parameter MREG =1;
parameter PREG =1;
parameter CARRYINREG =1;
parameter CARRYOUTREG =1;
parameter OPMODEREG =1;
parameter CARRYINSEL ="OPMODE5";
parameter B_INPUT ="DIRECT";
parameter RSTTYPE ="SYNC";
// DEFINE INPUTS
input [17:0] A,B,D,BCIN;
input [47:0] C,PCIN;
input [7:0] OPMODE;
input
CLK,CARRYIN,RSTA,RSTB,RSTC,RSTD,RSTM,RSTCARRYIN,RSTOPMODE,RSTP,CEA,CEB,CEC,CED,CECARYIN,CEM,C
EOPMODE,CEP;
// DEFINE OUTPUTS
output [17:0] BCOUT;
output [47:0] PCOUT,P;
output [35:0] M;
output CARRYOUT,CARRYOUTF;
// DEFINE INTERNAL WIRES
wire [17:0] A0_out,A1_out,B_out,B0_out,B1_out,D_out,Adder1_out,Adder1_mux_out;
wire [47:0] C_out,x_out,z_out,Adder_2_out,P_out;
wire [7:0] OPMODE_reg;
wire [35:0] mull_out,M_reg;
wire cout_ADDER,CI_reg,CI_mux,CARRYOUT_reg;
// INSTANTIATIONS

// A REG INSTANTIATION
Reg_Mux #(.width(18),.RSTTYPE(RSTTYPE)) A0_REG(A0REG,A,CLK,CEA,RSTA,A0_out);
Reg_Mux #(.width(18),.RSTTYPE(RSTTYPE)) A1_REG(A1REG,A0_out,CLK,CEA,RSTA,A1_out);
// B REG INSTANTIATION
Reg_Mux #(.width(18),.RSTTYPE(RSTTYPE)) B0_REG(B0REG,B_out,CLK,CEB,RSTB,B0_out);
Reg_Mux #(.width(18),.RSTTYPE(RSTTYPE)) B1_REG(B1REG,Adder1_mux_out,CLK,CEB,RSTB,B1_out);
// C REG INSTANTIATION
Reg_Mux #(.width(48),.RSTTYPE(RSTTYPE)) C_REG(CREG,C,CLK,CEC,RSTC,C_out);
// D REG INSTANTIATION
Reg_Mux #(.width(18),.RSTTYPE(RSTTYPE)) D_REG(DREG,D,CLK,CED,RSTD,D_out);

```

```

// M REG INSTANTIATION
Reg_Mux #(.width(36),.RSTTYPE(RSTTYPE)) M_REG(MREG,mull_out,CLK,CEM,RSTM,M_reg);
// CYI INSTANTIATION
Reg_Mux #(.width(1),.RSTTYPE(RSTTYPE))
CYI_REG(CARRYINREG,CI_mux,CLK,CECARYIN,RSTCARRYIN,CI_reg);
// CYO INSTANTIATION
Reg_Mux #(.width(1),.RSTTYPE(RSTTYPE))
CYO_REG(CARRYOUTREG,cout_ADDER,CLK,CECARYIN,RSTCARRYIN,CARRYOUT_reg);
// P REG INSTANTIATION
Reg_Mux #(.width(48),.RSTTYPE(RSTTYPE)) P_REG(PREG,Adder_2_out,CLK,CEP,RSTP,P_out);
// OPMODE REG INSTANTIATION
Reg_Mux #(.width(8),.RSTTYPE(RSTTYPE))
OPMODE_REG(OPMODEREG,OPMODE,CLK,CEOPMODE,RSTOPMODE,OPMODE_reg);

// SELECT THE INPUT OF B
assign B_out =(B_INPUT=="DIRECT")?B:(B_INPUT=="CASCADE")?BCIN:0;
// SELECT BETWEEN ADDATION & SUBTRACTION OPERATIONS AT THE FIRST ADDER
assign Adder1_out =(OPMODE_reg[6]==1)?D_out - B0_out:D_out + B0_out;
// SELECT THE OUTPUT OF THE MUX WHICH IS INFRONT OF THE FIRST ADDER
assign Adder1_mux_out = (OPMODE_reg[4]==1)?Adder1_out:B0_out;
// MULTIPLICATION
assign mull_out = B1_out * A1_out;
// SELECT THE OUTPUT OF MUX (X)
assign x_out=
(OPMODE_reg[1:0]==0)?48'b0:(OPMODE_reg[1:0]==1)?{12'b0,M_reg}:(OPMODE_reg[1:0]==2)?P_out:{D_o
ut[11:0],A1_out[17:0],B1_out[17:0]};
// SELECT THE OUTPUT OF MUX (Z)
assign z_out=
(OPMODE_reg[3:2]==0)?48'b0:(OPMODE_reg[3:2]==1)?PCIN:(OPMODE_reg[3:2]==2)?P_out:C_out;
// SELECT CARRY IN BETWEEN OPMODE[5] AND CARRY OUT OF ANOTHER DSP
assign CI_mux=(CARRYINSEL == "OPMODE5")?OPMODE_reg[5]:(CARRYINSEL ==
"CARRYIN")?CARRYIN:0;
// SELECT BETWEEN ADDATION & SUBTRACTION OPERATIONS AT THE SECOND ADDER
assign {cout_ADDER,Adder_2_out} = (OPMODE_reg[7]==1)?z_out - ( x_out + CI_reg ) : z_out
+ x_out + CI_reg;
// ASSIGN OUTPUTS
assign CARRYOUT = CARRYOUT_reg;
assign CARRYOUTF = CARRYOUT_reg;
assign BCOUT =B1_out;
assign PCOUT= P_out;
assign P = P_out ;
assign M = ~(~M_reg);

endmodule

```

- Testbench Code:

```

module DSP48A1_tb ();
    // DEFINE PARAMETERS
parameter A0REG_tb =0;
parameter A1REG_tb =1;
parameter B0REG_tb =0;
parameter B1REG_tb =1;
parameter CREG_tb =1;
parameter DREG_tb =1;
parameter MREG_tb =1;
parameter PREG_tb =1;
parameter CARRYINREG_tb =1;
parameter CARRYOUTREG_tb =1;
parameter OPMODEREG_tb =1;
parameter CARRYINSEL_tb ="OPMODE5";
parameter B_INPUT_tb ="DIRECT";
parameter RSTTYPE_tb ="SYNC";
// DEFINE INPUTS
reg [17:0] A_tb,B_tb,D_tb,BCIN_tb;
reg [47:0] C_tb,PCIN_tb;
reg [7:0] OPMODE_tb;
reg CLK_tb,CARRYIN_tb,RSTA_tb,RSTB_tb,RSTC_tb,RSTD_tb,RSTM_tb,RSTCARRYIN_tb
,RSTOPMODE_tb,RSTP_tb,CEA_tb,CEB_tb,CEC_tb,CED_tb,CECARYIN_tb,CEM_tb,CEOPMODE_tb,CEP_tb;
// DEFINE INSTANTIATION optputs
wire [17:0] BCOUT_dut;
wire [47:0] PCOUT_dut,P_dut;
wire [35:0] M_dut;
wire CARRYOUT_dut,CARRYOUTF_dut;
// DEFINE EXPECTED OUTPUT
reg [17:0] BCOUT_expected;
reg [47:0] PCOUT_expected,P_expected;
reg [35:0] M_expected;
reg CARRYOUT_expected,CARRYOUTF_expected;
// MODULE INSTANTIATION
DSP48A1
DUT(A_tb,B_tb,C_tb,D_tb,CARRYIN_tb,M_dut,P_dut,CARRYOUT_dut,CARRYOUTF_dut,CLK_tb,OPMODE_tb,
CEA_tb,CEB_tb,CEC_tb,CED_tb,CECARYIN_tb,CEM_tb,CEOPMODE_tb,CEP_tb,RSTA_tb,RSTB_tb,RSTC_tb,RST
D_tb
,RSTM_tb,RSTCARRYIN_tb,RSTOPMODE_tb,RSTP_tb,PCIN_tb,BCIN_tb,BCOUT_dut,PCOUT_dut);

integer i;
// CLOCK GENERATION
initial begin
    CLK_tb =0;
    forever begin
        #1 CLK_tb =~ CLK_tb;
    end
end
end

```

```

// DIRECTED Testbench
initial begin
    // ASSERT ALL RESET SIGNALS
    RSTA_tb = 1;
    RSTB_tb = 1;
    RSTC_tb = 1;
    RSTD_tb = 1;
    RSTM_tb = 1;
    RSTCARRYIN_tb = 1;
    RSTOPMODE_tb = 1;
    RSTP_tb = 1;
    // ENABLE ALL NECESSARY CLOCK ENABLES
    CEA_tb = 1;
    CEB_tb = 1;
    CEC_tb = 1;
    CED_tb = 1;
    CECARYIN_tb = 1;
    CEM_tb = 1;
    CEOPMODE_tb = 1;
    CEP_tb = 1;
    // INITIALIZE ALL INPUT SIGNALS TO ZERO
    A_tb = 0;
    B_tb = 0;
    C_tb = 0;
    D_tb = 0;
    PCIN_tb = 0;
    BCIN_tb = 0;
    CARRYIN_tb = 0;
    OPMODE_tb = 0;
    // INITIALIZE ALL EXPECTED OUTPUT VALUES TO ZERO
    P_expected = 0;
    M_expected = 0;
    CARRYOUT_expected = 0;
    CARRYOUTF_expected = 0;
    BCOUT_expected = 0;
    PCOUT_expected = 0;

    @(negedge CLK_tb);

    // RELEASE ALL RESET SIGNALS
    RSTA_tb = 0;
    RSTB_tb = 0;
    RSTC_tb = 0;
    RSTD_tb = 0;
    RSTM_tb = 0;
    RSTCARRYIN_tb = 0;
    RSTOPMODE_tb = 0;
    RSTP_tb = 0;
    for(i=0;i<99;i=i+1)begin
        OPMODE_tb =$random;
    end
end

```



```

A_tb = $urandom_range(1,500);
B_tb = $urandom_range(1,500);
C_tb = $urandom_range(1,500);
D_tb = $urandom_range(1,500);
PCIN_tb = $urandom_range(1,500);
BCIN_tb = $urandom_range(1,500);
CARRYIN_tb = $random;
    repeat(3) @(negedge CLK_tb);
// TEST BOUT OUTPUT
if(OPMODE_tb[4])begin
    if(OPMODE_tb[6])
        BCOUT_expected = D_tb - B_tb;
    else
        BCOUT_expected = D_tb + B_tb;
end
else begin
    BCOUT_expected = B_tb;
end
// TEST MULTIPLICATION OUTPUT
M_expected = BCOUT_expected * A_tb;
#20;
if((M_expected != M_dut) || (BCOUT_expected != BCOUT_dut))begin
    $display("Error");
    $stop;
end
end
// TEST P AND CARRYOUT AT OPMODE 0000_0010
OPMODE_tb = 2;
for(i=0;i<49;i=i+1)begin
    A_tb = $urandom_range(1,500);
    B_tb = $urandom_range(1,500);
    C_tb = $urandom_range(1,500);
    D_tb = $urandom_range(1,500);
    PCIN_tb = $urandom_range(1,500);
    BCIN_tb = $urandom_range(1,500);
    {CARRYOUT_expected,P_expected} = P_expected;
    repeat(4) @(negedge CLK_tb);
    if((P_expected != P_dut) && (CARRYOUT_expected != CARRYOUT_dut))begin
        $display("Error");
        $stop;
    end
end
// TEST P AND CARRYOUT WHEN OUTPUT OF X_MUX IS {D_tb[11:0],A_tb,B_tb} AND Z_MUX IS ZERO
OPMODE_tb = 3;
for(i=0;i<49;i=i+1)begin
    A_tb = $urandom_range(1,500);
    B_tb = $urandom_range(1,500);
    C_tb = $urandom_range(1,500);
    D_tb = $urandom_range(1,500);
    PCIN_tb = $urandom_range(1,500);

```

```

BCIN_tb = $urandom_range(1,500);
{CARRYOUT_expected,P_expected} = {D_tb[11:0],A_tb,B_tb};
repeat(4) @(negedge CLK_tb);
if((P_expected != P_dut) && (CARRYOUT_expected != CARRYOUT_dut))begin
    $display("Error");
    $stop;
end
end
// TEST P AND CARRYOUT WHEN OUTPUT OF X_MUX IS ZERO AND Z_MUX IS ZERO
OPMODE_tb = 0;
for(i=0;i<49;i=i+1)begin
    A_tb = $urandom_range(1,500);
    B_tb = $urandom_range(1,500);
    C_tb = $urandom_range(1,500);
    D_tb = $urandom_range(1,500);
    PCIN_tb = $urandom_range(1,500);
    BCIN_tb = $urandom_range(1,500);

    {CARRYOUT_expected,P_expected} = 0;

    repeat(4) @(negedge CLK_tb);
    if((P_expected != P_dut) && (CARRYOUT_expected != CARRYOUT_dut))begin
        $display("Error");
        $stop;
    end
end
// TEST P AND CARRYOUT WHEN OUTPUT OF X_MUX IS MULTIPLICATION AND Z_MUX IS ZERO
OPMODE_tb = 1;
for(i=0;i<49;i=i+1)begin
    A_tb = $urandom_range(1,500);
    B_tb = $urandom_range(1,500);
    C_tb = $urandom_range(1,500);
    D_tb = $urandom_range(1,500);
    PCIN_tb = $urandom_range(1,500);
    BCIN_tb = $urandom_range(1,500);
    if(OPMODE_tb[4])begin
        if(OPMODE_tb[6])
            BCOUT_expected = D_tb - B_tb;
        else
            BCOUT_expected = D_tb + B_tb;
    end
    else begin
        BCOUT_expected = B_tb;
    end
    M_expected = BCOUT_expected * A_tb;
    {CARRYOUT_expected,P_expected} = M_expected;
    repeat(4) @(negedge CLK_tb);
    if((P_expected != P_dut) && (CARRYOUT_expected != CARRYOUT_dut))begin
        $display("Error");
        $stop;
    end
end

```

```

        end

    end

    // TEST P AND CARRYOUT WHEN OUTPUT OF X_MUX IS ZERO AND Z_MUX IS PCIN
    OPMODE_tb = 8'b0000_0100;
    for(i=0;i<49;i=i+1)begin
        A_tb = $urandom_range(1,500);
        B_tb = $urandom_range(1,500);
        C_tb = $urandom_range(1,500);
        D_tb = $urandom_range(1,500);
        PCIN_tb = $urandom_range(1,500);
        BCIN_tb = $urandom_range(1,500);
        {CARRYOUT_expected,P_expected} = PCIN_tb;
        repeat(4) @(negedge CLK_tb);
        if((P_expected != P_dut) && (CARRYOUT_expected != CARRYOUT_dut))begin
            $display("error");
            $stop;
        end
    end

    end

    // TEST P AND CARRYOUT WHEN OUTPUT OF X_MUX IS ZERO AND Z_MUX IS C
    OPMODE_tb = 8'b0000_1100;
    for(i=0;i<49;i=i+1)begin
        A_tb = $urandom_range(1,500);
        B_tb = $urandom_range(1,500);
        C_tb = $urandom_range(1,500);
        D_tb = $urandom_range(1,500);
        PCIN_tb = $urandom_range(1,500);
        BCIN_tb = $urandom_range(1,500);
        {CARRYOUT_expected,P_expected} = C_tb;
        repeat(4) @(negedge CLK_tb);
        if((P_expected != P_dut) && (CARRYOUT_expected != CARRYOUT_dut))begin
            $display("error");
            $stop;
        end
    end

    end

    $stop;
end

initial begin
    $monitor("A=%d,B=%d,C=%d,D=%d,BCOUT=%d,M=%d,P=%d,P_dut=%d",A_tb,B_tb,C_tb,D_tb,BCOUT_expected,M_expected,P_expected,P_dut);
end

endmodule

/*case (OPMODE_tb[1:0])
    0:X_MUX=0;
    1:X_MUX=M_expected;
    2:X_MUX=P_expected;
    3:X_MUX={D_tb[11:0],A_tb[17:0],B_tb[17:0]};
endcase



```

```
case (OPMODE_tb[3:2])
    0:Z_MUX=0;
    1:Z_MUX=PCIN_tb;
    2:Z_MUX=P_expected;
    3:Z_MUX=C_tb;
endcase


if(OPMODE_tb[7])begin
    if(CARRYINSEL_tb == "OPMODE5")
        {CARRYOUT_expected,P_expected} = Z_MUX - (X_MUX + OPMODE_tb[5]);
    else if(CARRYINSEL_tb == "CARRYIN")
        {CARRYOUT_expected,P_expected} = Z_MUX - (X_MUX + CARRYIN_tb );
    end
else begin
    if(CARRYINSEL_tb == "OPMODE5")
        {CARRYOUT_expected,P_expected} = Z_MUX + (X_MUX + OPMODE_tb[5] );
    else if(CARRYINSEL_tb == "CARRYIN")
        {CARRYOUT_expected,P_expected} = Z_MUX + (X_MUX + CARRYIN_tb );
    end*/
end*/
```

  4. Simulation Tool:


- DO File:
vlib work
vlog REG_MUX.v DSP.v DSP_tb.v
vsim -voptargs=+acc work.DSP48A1_tb
add wave *
run -all
//quit -sim
- Wave Form:
 - Test M & BOUT outputs




- Test P at opcode = 0

 

 
- Test P & CARRYOUT when outputs of X_MUX is {D_tb[11:0],A,B} and Z_MUX is zero



 
- Test P & CARRYOUT when output of X_MUX is zero and Z_MUX is zero:



 
- Test P & CARRYOUT when output of X_MUX is M and Z_MUX is zero:



 - Test P & CARRYOUT when output of X_MUX is 0 and Z_MUX is PCIN:



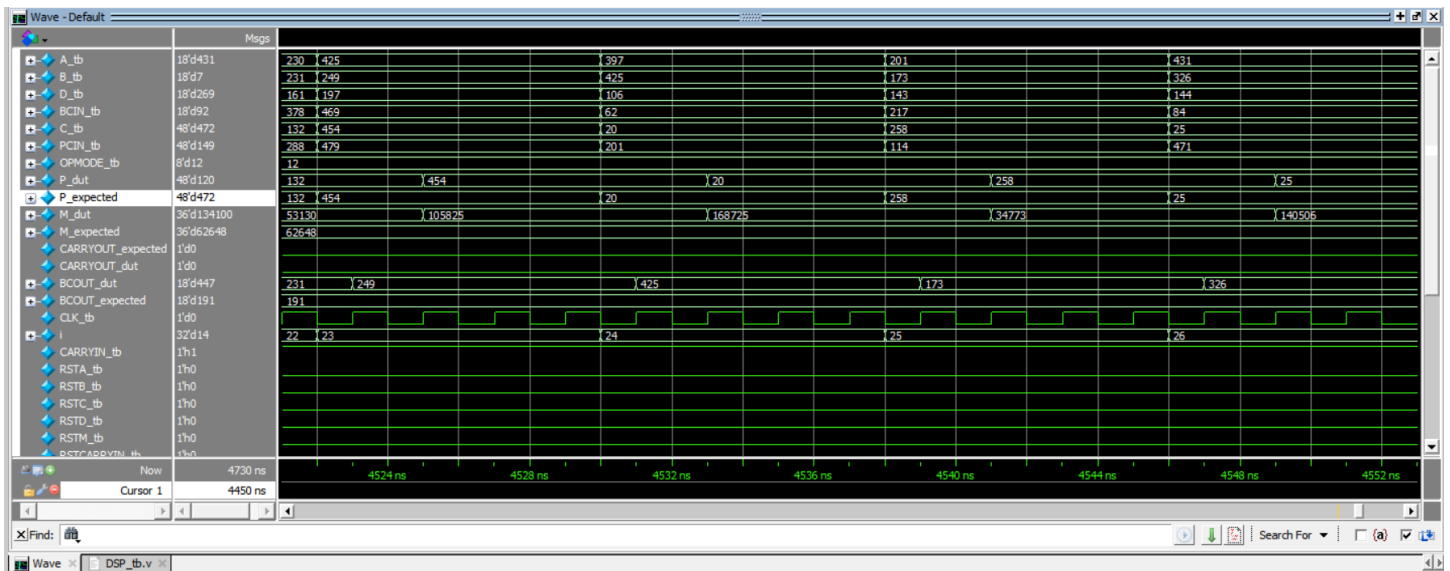- Test P & CARRYOUT when output of X_MUX is 0 and Z_MUX is C:



5. Synthesis Tool:


- Constraint File:

```
## Clock signal
set_property -dict {PACKAGE_PIN W5 IOSTANDARD LVCMOS33} [get_ports CLK]
create_clock -period 10.000 -name sys_clk_pin -waveform {0.000 5.000} -add [get_ports CLK]

## Configuration options, can be used for all designs
set_property CONFIG_VOLTAGE 3.3 [current_design]
set_property CFGBVS VCC0 [current_design]

## SPI configuration mode options for QSPI boot, can be used for all designs
set_property BITSTREAM.GENERAL.COMPRESS TRUE [current_design]
set_property BITSTREAM.CONFIG.CONFIGRATE 33 [current_design]
set_property CONFIG_MODE SPIx4 [current_design]
```

- Elaboration Messages & Schematic:

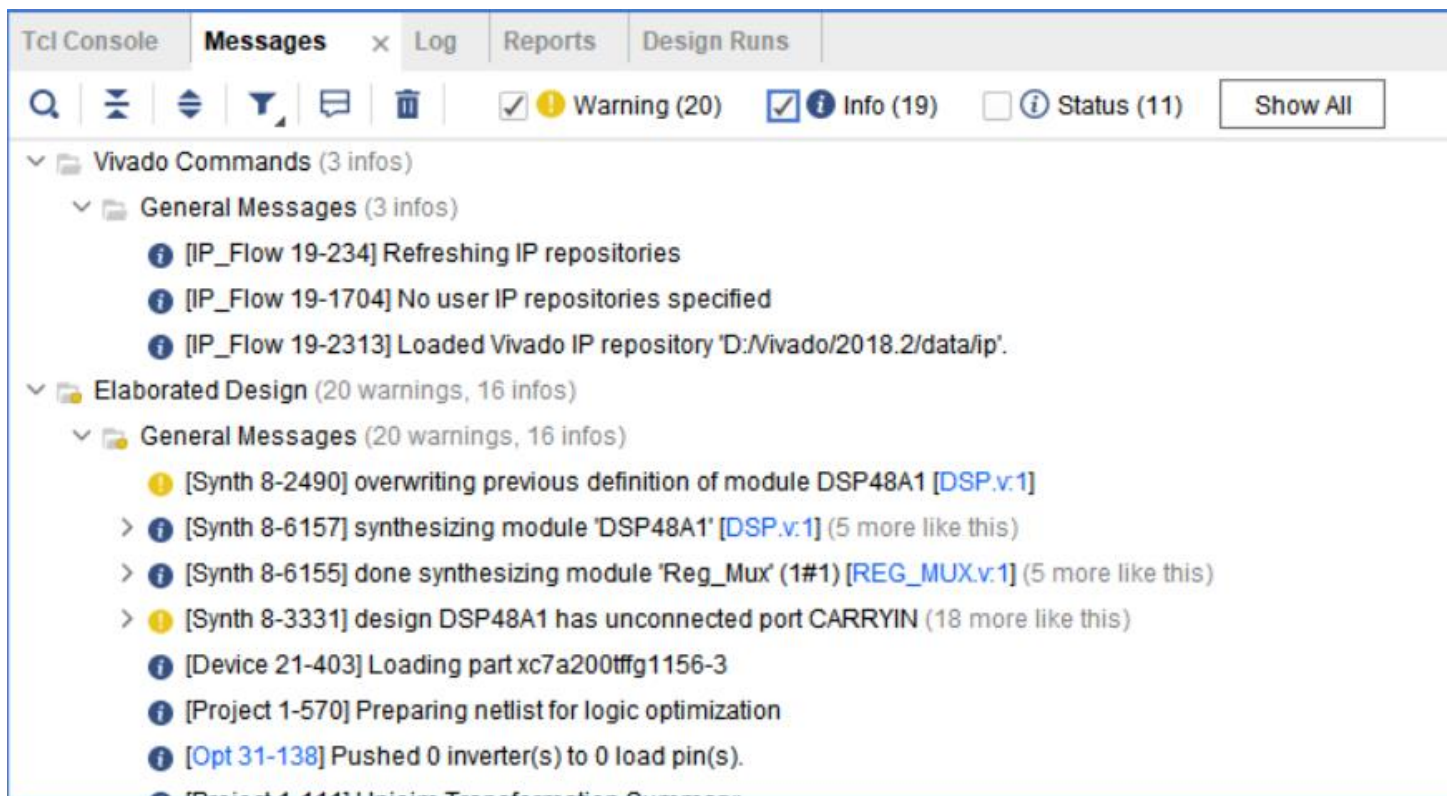

The screenshot displays the Vivado IDE's Messages window, which is organized into tabs: Tcl Console, Messages (selected), Log, Reports, and Design Runs. The Messages tab shows a hierarchical list of messages. Under 'Vivado Commands (3 infos)', there are 'General Messages (3 infos)' including refreshing IP repositories, no user IP repositories specified, and loading the Vivado IP repository. Under 'Elaborated Design (20 warnings, 16 infos)', there are 'General Messages (20 warnings, 16 infos)' including a warning about overwriting the module DSP48A1, synthesizing and done synthesizing modules 'DSP48A1' and 'Reg_Mux', a warning about an unconnected port CARRYIN, and information about loading the device part, preparing the netlist, and pushing inverters.

Tcl Console **Messages** x Log Reports Design Runs

🔍 ⚙️ ⚡ 🗑️ 🗑️ ☒ ⚠️ Warning (20) ☒ ⓘ Info (19) ☐ ⓘ Status (11) Show All

▼ 📁 Vivado Commands (3 infos)

 ▼ 📁 General Messages (3 infos)

 ⓘ [IP_Flow 19-234] Refreshing IP repositories

 ⓘ [IP_Flow 19-1704] No user IP repositories specified

 ⓘ [IP_Flow 19-2313] Loaded Vivado IP repository 'D:/Vivado/2018.2/data/ip'.

▼ 📁 Elaborated Design (20 warnings, 16 infos)

 ▼ 📁 General Messages (20 warnings, 16 infos)

 ⚠️ [Synth 8-2490] overwriting previous definition of module DSP48A1 [DSP.v:1]

 > ⓘ [Synth 8-6157] synthesizing module 'DSP48A1' [DSP.v:1] (5 more like this)

 > ⓘ [Synth 8-6155] done synthesizing module 'Reg_Mux' (1#1) [REG_MUX.v:1] (5 more like this)


 > ⚠️ [Synth 8-3331] design DSP48A1 has unconnected port CARRYIN (18 more like this)

 ⓘ [Device 21-403] Loading part xc7a200tffg1156-3

 ⓘ [Project 1-570] Preparing netlist for logic optimization

 ⓘ [Opt 31-138] Pushed 0 inverter(s) to 0 load pin(s).

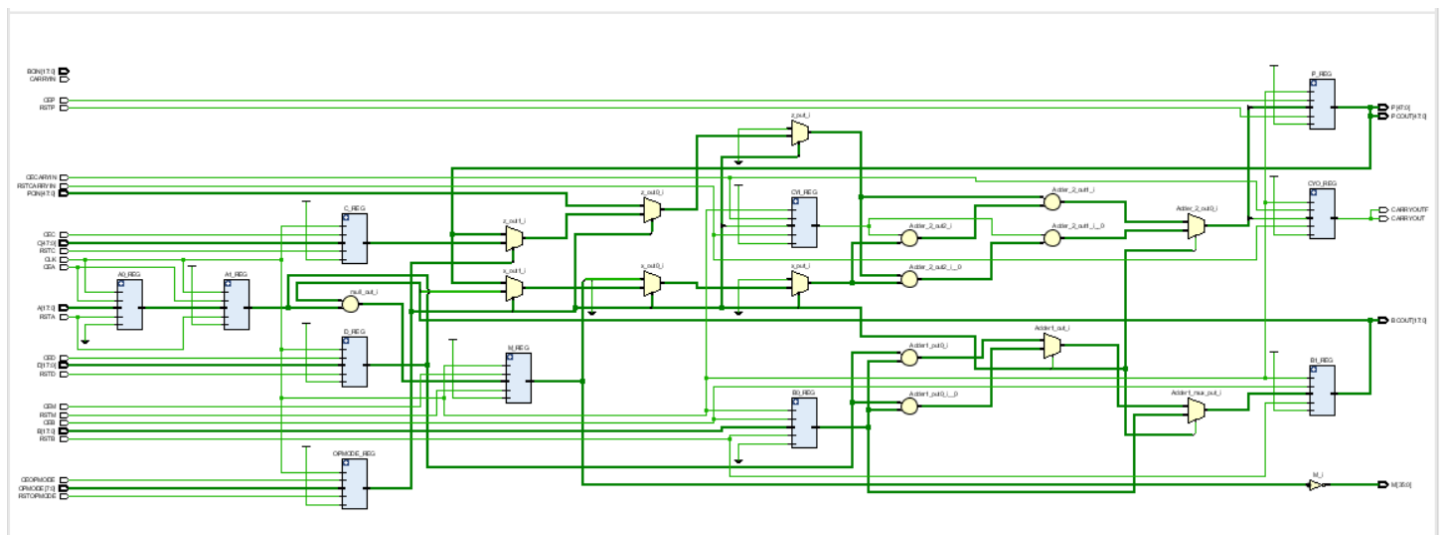 ⓘ [Project 1-441] Uniquing Transformation Summary



- Synthesis Messages, Utilization report, timing report & Schematic snippets:

Tcl Console Messages x Log Reports Design Runs Debug

Warning (58) Info (57) Status (19) Show All

[Common 17-83] Releasing license. Synthesis

[Constraints 18-5210] No constraint will be written out.

[Common 17-1381] The checkpoint 'C:/Users/Mohamed/OneDrive/Desktop/Digital Design/project/project_1/project_1.runs/synth_1/DSP48A1.dcp' has been generated.

[runtcl-4] Executing : report_utilization -file DSP48A1_utilization_synth.rpt -pb DSP48A1_utilization_synth.pb

[Common 17-206] Exiting Vivado at Sat Mar 8 02:36:35 2025...

✓ Synthesized Design (6 infos)

✓ General Messages (6 infos)

[Netlist 29-17] Analyzing 207 Unisim elements for replacement

[Netlist 29-28] Unisim Transformation completed in 1 CPU seconds

[Project 1-479] Netlist was created with Vivado 2018.2

[Project 1-570] Preparing netlist for logic optimization

[Opt 31-138] Pushed 0 inverter(s) to 0 load pin(s).



[Project 1-111] Unisim Transformation Summary:
No Unisim elements were transformed.


Name	Slice LUTs (134600)	Slice Registers (269200)	DSP s (740)	Bonded IOB (500)	BUFGCTRL (32)
✓ N DSP48A1	230	160	1	327	1
✖ A1_REG (Reg_Mux)	0	18	0	0	0
✖ B1_REG (Reg_Mux_0)	0	18	0	0	0
✖ C_REG (Reg_Mux__p...	0	48	0	0	0
✖ CYI_REG (Reg_Mux__...	1	1	0	0	0
✖ CYO_REG (Reg_Mux__...	0	1	0	0	0
✖ D_REG (Reg_Mux_2)	0	18	0	0	0
✖ OPMODE_REG (Reg_...	228	8	0	0	0
✖ P_REG (Reg_Mux__p...	0	48	0	0	0

Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 5.168 ns	Worst Hold Slack (WHS): 0.182 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 106	Total Number of Endpoints: 106	Total Number of Endpoints: 162

  All user specified timing constraints are met.



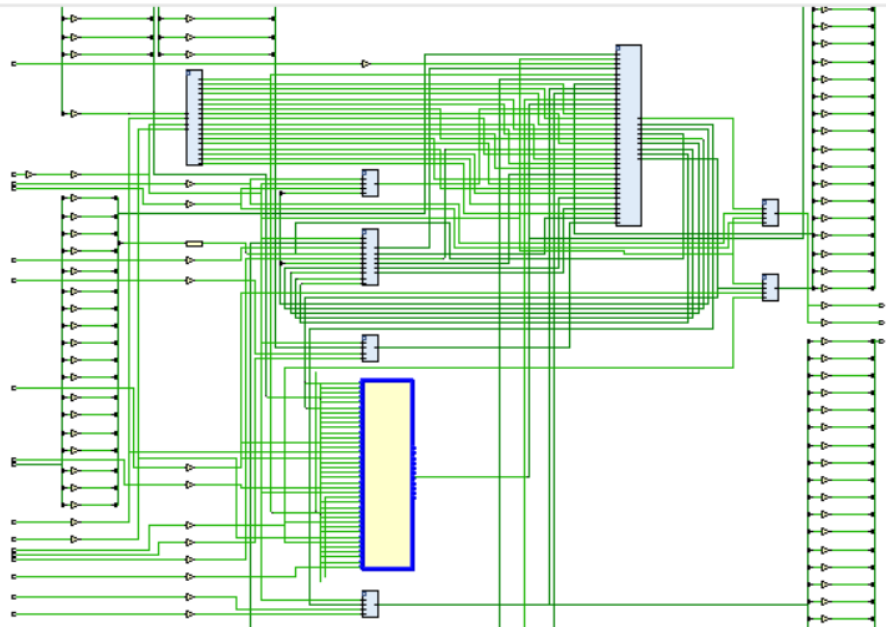

- Implementation Messages, Utilization report, timing report & device snippets

Tcl Console
Messages
Log
Reports
Design Runs
Power
DRC
Methodology
Timing
? _ □ □

Warning (60)
Info (242)
Status (459)
Show All

[Device 21-403] Loading part xc7a200tffg1156-3

[Project 1-236] Implementation specific constraints were found while reading constraint file [C:/Users/Mohamed/OneDrive/Desktop/Digital Design/project/Constraints/_basys3.xdc]. These constraints will be ignored for synthesis but will be used in implementation. Impacted constraints are listed in the file [X:/DSP48A1_prop1mpl.xdc]. Resolution: To avoid this warning, move constraints listed in [Undefined] to another XDC file and exclude this new file from synthesis with the used_in_synthesis property (File Properties dialog in GUI) and re-run elaboration/synthesis.

[Synth 8-5818] HDL ADVISOR - The operator resource <adder> is shared. To prevent sharing consider applying a KEEP on the output of the operator [DSP.v:61] (1 more like this)

[Synth 8-3886] merging instance 'A0_REG/out_reg_reg[0]' (FDRE) to 'A1_REG/out_reg_reg[0]' (17 more like this)

[Synth 8-3332] Sequential element (B0_REG/out_reg_reg[17]) is unused and will be removed from module DSP48A1. (17 more like this)

[Synth 8-5842] Cannot pack DSP OPMODE registers because of constant '1' value. Packing the registers will cause simulation mismatch at initial cycle [DSP.v:65]

[Project 1-571] Translating synthesized netlist

[Netlist 29-17] Analyzing 207 Unisim elements for replacement

[Netlist 29-28] Unisim Transformation completed in 0 CPU seconds

[Project 1-570] Preparing netlist for logic optimization (1 more like this)

[Opt 31-138] Pushed 0 inverter(s) to 0 load pin(s).

[Project 1-111] Unisim Transformation Summary:
No Unisim elements were transformed. (4 messages like this)

Name	Slice LUTs (133800)	Slice Registers (267600)	F7 Muxes (66900)	F8 Muxes (33450)	Slice (33450)	LUT as Logic (133800)	LUT as Memory (46200)	LUT Flip Flop Pairs (133800)	Block RAM Tile (365)	DSP s (740)
▼ N DSP48A1	2615	3986	64	5	1466	2190	425	1493	6.5	1
<input checked="" type="checkbox"/> A1_REG (Reg_Mux)	0	18	0	0	6	0	0	0	0	0
<input checked="" type="checkbox"/> B1_REG (Reg_Mux_0)	0	18	0	0	6	0	0	0	0	0
<input checked="" type="checkbox"/> C_REG (Reg_Mux_p...	0	48	0	0	12	0	0	0	0	0
<input checked="" type="checkbox"/> CYI_REG (Reg_Mux_...	1	1	0	0	1	1	0	1	0	0
<input checked="" type="checkbox"/> CYO_REG (Reg_Mux_...	0	1	0	0	1	0	0	0	0	0
<input checked="" type="checkbox"/> D_REG (Reg_Mux_2)	0	18	0	0	10	0	0	0	0	0
> <input checked="" type="checkbox"/> dbg_hub (dbg_hub)	476	727	0	0	252	452	24	303	0	0
<input checked="" type="checkbox"/> OPCODE_REG (Reg_...	228	8	0	0	67	228	0	0	0	0

